# CPU Implementation Project



**Crawford James & Quinn Ramsay** 





## The ALU

#### **Input Design:**


• Created two 32-bit input pins to visualize effectiveness and verify outputs.

#### Implementation:

- Connected input pins to an arithmetic or gate.
- Linked the gates output to the inputs of a multiplexer for selection of arithmetic.
- Connected the multiplexer to a 32-bit output pin.
- Used a 3-bit selector pin to control the multiplexer.
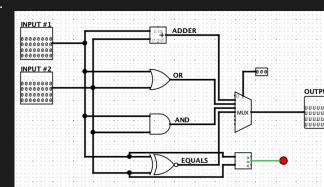
#### **Equality Operation:**

- Used an XNOR gate to send an output to the multiplexer for processing.
- Connected original inputs to a comparator.
- Linked the comparator to an LED output to indicate equality.



—

## The Register File

#### Input


- 8 register banks with 8 bit wide paths for each.
- Decoder used to determine which register to write to based on the address input.
- Two different read addresses to access data simultaneously.

#### **Implementation**

- Each register receives data through a sharded bus controlled by the decoder and write enabler.
- Multiplexer to select the output from the correct register.
- Two multiplexers help with simultaneous outputs from the register file.
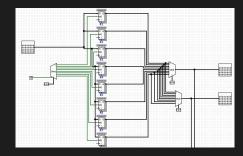
#### Output

- Both selected register outputs are connected to 8-bit output pins.
- Ensure correct read/write operation through control signals.





—

# Testing The Program

#### **Testing Setup:**

• Assigned separate 32-bit input and output pins for the Register File and ALU to visualize issues.

#### **Independent Testing:**


• Built and tested each component separately to confirm functionality.

#### **Integration Testing:**

• Combined both components and verified output accuracy.
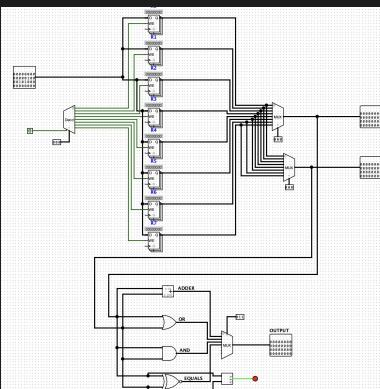
#### **Verification Process:**

- Input random binary numbers and tested different values.
- Ensured outputs remained consistent across all cases.



\_\_

### **Problems We Encountered**

#### ALU:

- Designing the equality operation was the most difficult part.
- Required trial and error to determine the correct arithmetic function or logic gate.

#### **Register File**

- Figuring out how we wanted to use the registers. Specifically addressing the correct register for read and write.
- Making sure that writing only happens at the right time given.

—

## Real World Application

#### **Role of ALU and Register File:**

Essential components of modern CPUs for fast and efficient data processing.

#### **ALU in Real-World CPUs:**

• CPUs use multiple ALUs in parallel for complex tasks like graphics processing and floating-point math.

#### **Function of the Register File:**

• Stores data for quick access, reducing the need to retrieve it from slower memory.

#### **Performance Optimizations:**

• Techniques like pipelining and out-of-order execution enhance speed and efficiency.

#### Impact on Technology:

Improves performance in devices ranging from gaming PCs to smartphones and embedded systems.





